
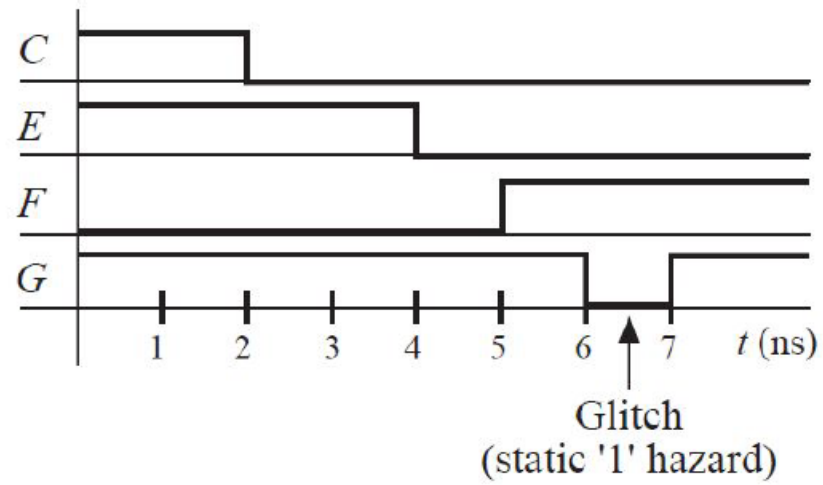


8.3 (a)

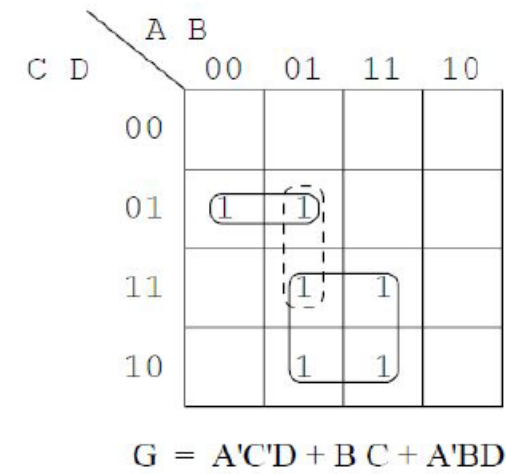

8.3 (b) Modified circuit (to avoid hazards)



8.4 $A = 1; B = \mathbf{Z}; C = 1 \cdot \mathbf{Z} = \mathbf{X}; D = 1 + \mathbf{Z} = 1;$
 $E = \mathbf{X}' = \mathbf{X}; F = 1' = 0; G = \mathbf{X} \cdot 0 = 0;$
 $H = \mathbf{X} + 0 = \mathbf{X}$

See FLD Table 8-1, p. 241.


8.5

$$A = B = 0, C = D = 1$$

$$\text{So } F = AB'D + BC'D' + BCD = 0$$

But in the figure, gate 4 outputs $F = 1$, indicating something is wrong. For the last NAND gate, $F = 0$ only when all its inputs are 1. But the output of gate 3 is 0. Therefore, gate 4 is working properly, but gate 3 is connected incorrectly or is malfunctioning.

8.10

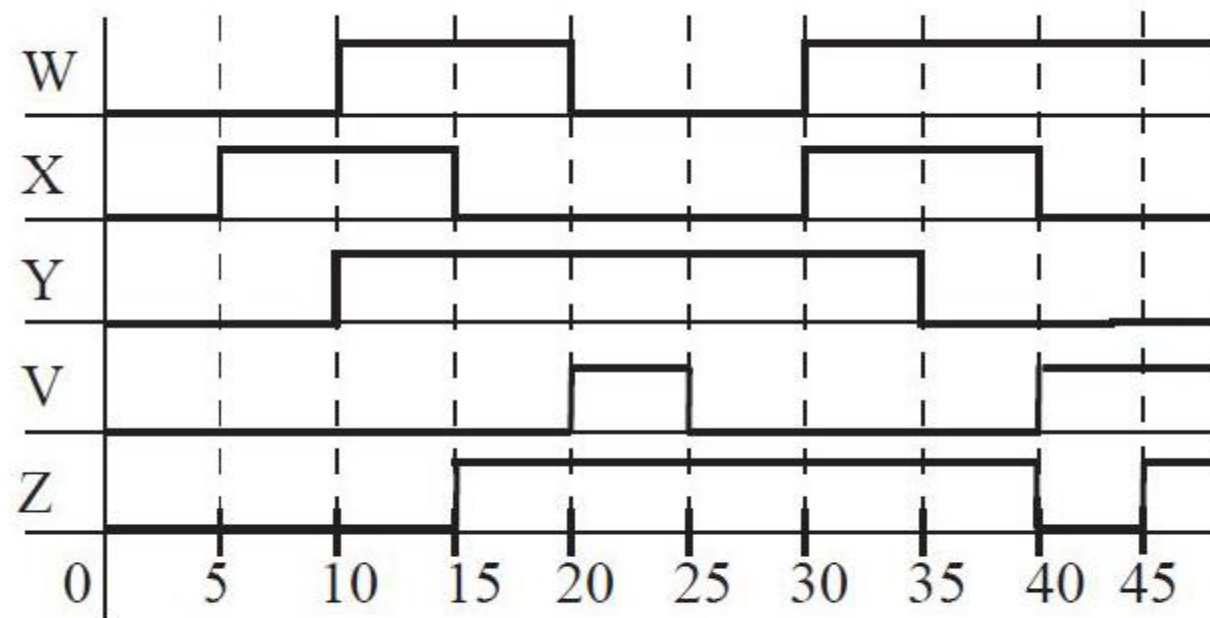

8.16 (a) $F(A, B, C, D) = \sum m(0, 2, 5, 6, 7, 8, 9, 12, 13, 15)$

There are 3 different minimum AND-OR solutions to this problem. The problem asks for any two of these.

		A B			
		00	01	11	10
C D	00	1		1	1
	01		1	1	1
	11		1	1	
	10	1	1		

$$F = BD + AC' + A'CD' + B'C'D'$$

Solution 1: 1-hazards are between
 $0000 \leftrightarrow 0010$ and $0111 \leftrightarrow 0110$

		A B			
		00	01	11	10
C D	00	1		1	1
	01		1	1	1
	11		1	1	
	10	1	1		

$$F = BD + AC' + A'B'D' + A'BC$$

Solution 2: 1-hazards are between
 $0010 \leftrightarrow 0110$ and $0000 \leftrightarrow 1000$

		A B			
		00	01	11	10
C D	00	1		1	1
	01		1	1	1
	11		1	1	
	10	1	1		

$$F = BD + AC' + A'B'D' + A'CD'$$

Solution 3: 1-hazards are between
 $0111 \leftrightarrow 0110$ and $0000 \leftrightarrow 1000$

Without hazards: $F' = BD + AC' + B'C'D' + A'CD' + A'B'D' + A'BC$

8.16 (b)

		A B			
		00	01	11	10
C D	00		0		
	01	0			
	11	0			0
	10			0	0

$$F = (A + B + D') (A + B' + C + D) (A' + C' + D) (A' + B + C')$$

0-hazard is between 1011 \leftrightarrow 0011

Either way, without hazard:

$$F' = (A + B + D') (A + B' + C + D) (A' + C' + D) (B + C' + D') (A' + B + C')$$

		A B			
		00	01	11	10
C D	00		0		
	01	0			
	11	0			0
	10			0	0

$$F = (A + B + D') (A + B' + C + D) (A' + C' + D) (B + C' + D')$$

0-hazard is between 1011 \leftrightarrow 1010

8.A

$ABCD$	X_1	X_2	X_3	X_4	X_5	X_6	X_7
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	0	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1

$$X_1 = B'D' + B D + A + C D = \underline{B'D'} + \underline{BC'D} + A + \underline{CD} \text{ (used in circuit)}$$

$$X_1 = B'D' + B D + A + B'C$$

$$X_2 = B' + \underline{C'D'} + \underline{CD}$$

$$X_3 = C' + D + B$$

$$X_4 = \underline{B'D'} + \underline{B'C} + \underline{B C'D} + \underline{C D'}$$

$$X_5 = \underline{B'D'} + \underline{C D'}$$

$$X_6 = \underline{C'D'} + \underline{B C'} + B D' + A$$

$$X_7 = \underline{B'C} + \underline{B C'} + A + \underline{C D'} \text{ (used in circuit)}$$

$$X_7 = B'C + B C' + A + B D'$$

This solution uses 15 gates and 41 gate inputs.

Students are allowed to use a maximum of 18 gates.